

# Electrical and Electromechanical Computer Science


Current  $\rightarrow$  voltage  $\rightarrow$  Resistance

$$V = I/R$$

## Band Colours


Tolerance values

Black - $0, 10^0$	silver - $\pm 10\%$	NA
Brown - $1, 10^1$		$\pm 1$
Red - $2, 10^2$		$\pm 2$
Orange - $3, 10^3$		NA
Yellow - $4, 10^4$		NA
Green - $5, 10^5$	blue - $6, 10^6$	$\pm 0.5\%$
Violet - $7, 10^7$		$\pm 0.25\%$
Grey - $8, 10^8$		$\pm 0.10\%$
White - $9, 10^9$		NA $\pm 0.05\%$
Gold - $10^{\pm 10}$	$\pm 5\%$	NA

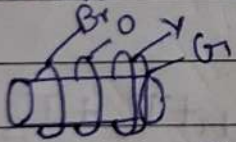

Brown - 1, Orange 3, Yellow -  $10^4$ , Gold -  $\pm 5$

$$13 \times 10^4 \pm 5$$

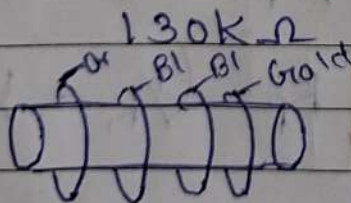


$$30 \times 10^0 \pm 5$$

$$= 30 \Omega \pm 5 //$$


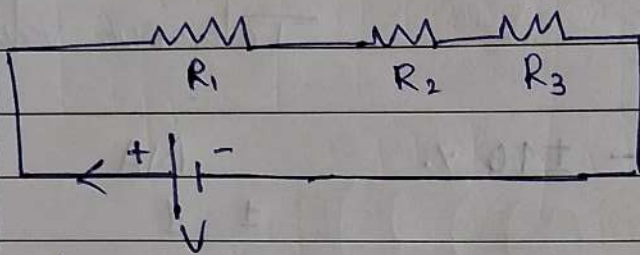
## Resistors in Series

Current - remains Same  
Voltage - changes



$$V = V_1 + V_2 + V_3$$


$$IR_s = IR_1 + IR_2 + IR_3$$

$$IR_s = I(R_1 + R_2 + R_3)$$

$$\Rightarrow R_s = R_1 + R_2 + R_3$$
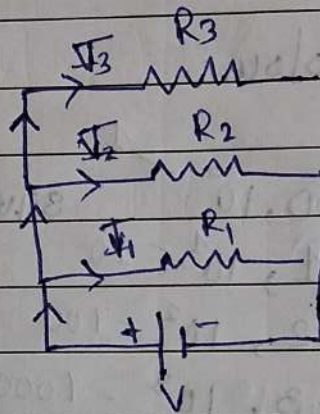
## Resistors in Parallel

Current - changes  
Voltage - Remains Same



$$I = V/R$$

$$I = V/R$$

$$V/R_1 = I_1$$

$$V/R_2 = I_2$$

$$V/R_3 = I_3$$

$$I = I_1 + I_2 + I_3$$

$$V/R_p = V/R_1 + V/R_2 + V/R_3$$

$$V/R_p = V(1/R_1 + 1/R_2 + 1/R_3)$$


$$R_p = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$



07/5/10

# Diodes

## PN junction diode

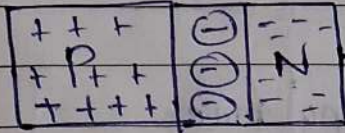


P and N subscript

particles

P- Holes containing protons, relectrons and neutrons, whereas as

N- ~~A~~ Electron are negatively charged

\* Holes are heavy than electrons

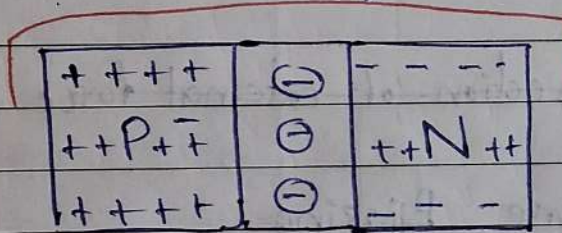

Barrier potential

(due to dis. electrons + holes stop move)

PN junction



\* opposite. poles attract each other

pulling

\* positive carriers are heavy compared to electrons

\* Electrons move faster

Re combination of electrons → Biasing

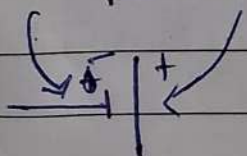
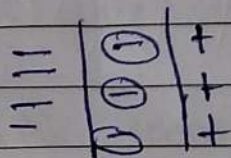


electrostatic field

P type → Anode

N type → Cathode




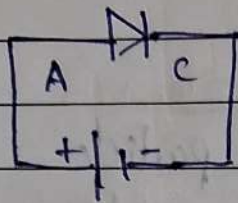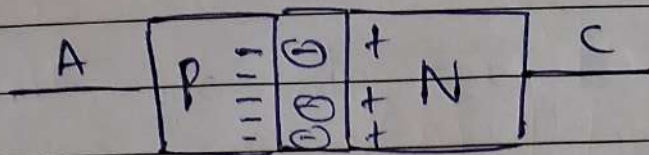


Connection of external force

Electron + holes is called Biasing

Forward Biasing

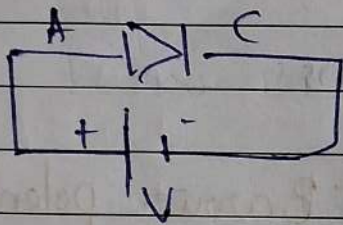

Connection of external force

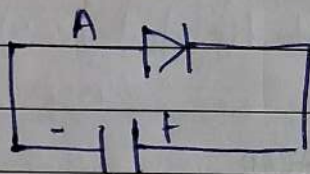


Reverse Biasing :

(-)  $P \rightarrow A$


(+)  $N \rightarrow C$

Forward Bias:

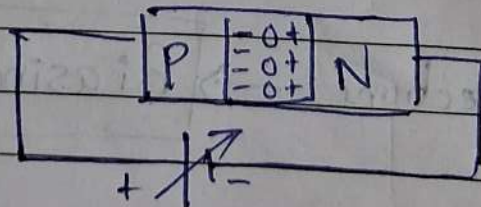

Silicon material (Si)  $V_{Bp} \rightarrow 0.7v$

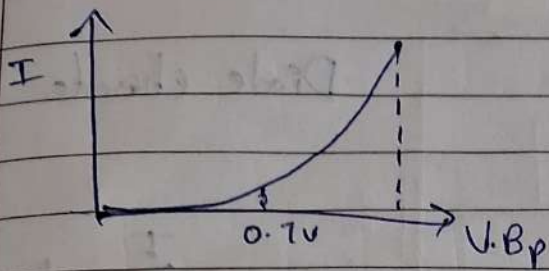Germanium " " (Ge)  $V_{Bp} \rightarrow 0.3v$




Diode is unidirectional

here  $I$  - movement of both carriers  
so it is called as Bipolar device  
 $\therefore$  diode is bipolar device

The Direction of current ( $I$ )

Anode to cathode (so it is unidirectional)

Reverse Biasing

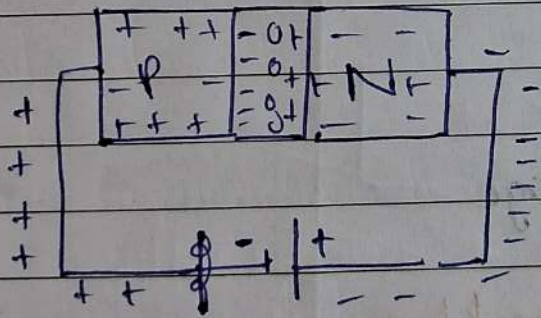

$\times$  -ve plate  $\rightarrow$  p layer majority  $\rightarrow$  +ve attract


+ve plate  $\rightarrow$  N layer majority  $\rightarrow$  -ve attract

$\therefore$  No carriers crossing the junction


$\therefore I = 0$



⇒ At one stage

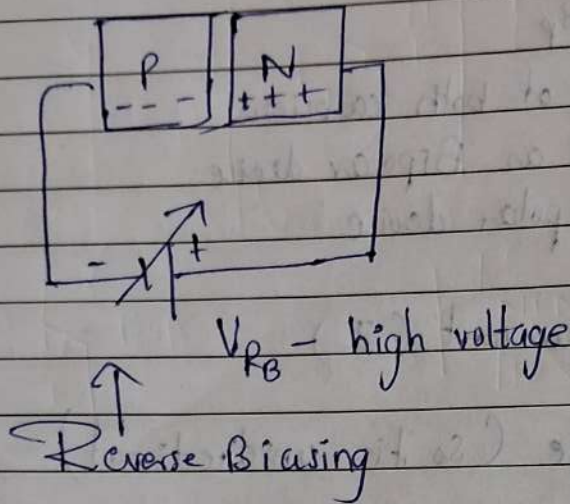

Diode character

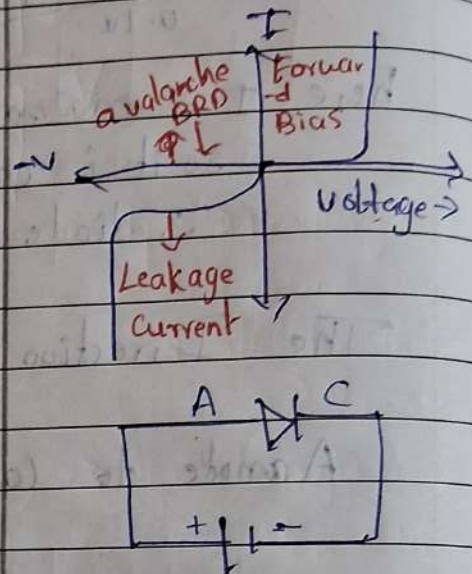


due to high potential  
→ high force moving the charges



electrons (-) → N layer  
protons (+) → P layer

∴ due to this function damage  
This damage is called  
Avalanche Breakdown

## CHARACTERISTICS

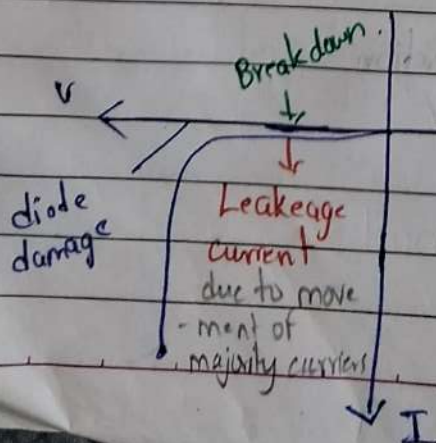

# Zener Diode

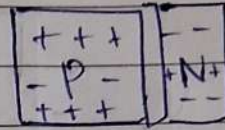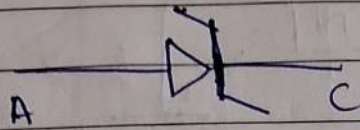




Zener Diode

- Very thin PN junction layer
- Zener diode is Bi directional
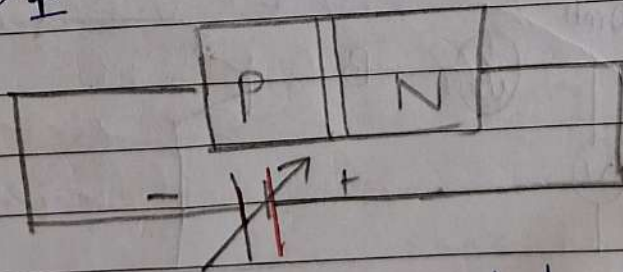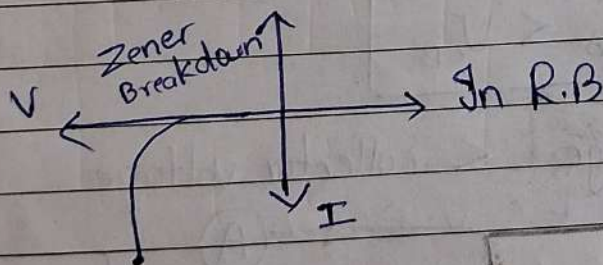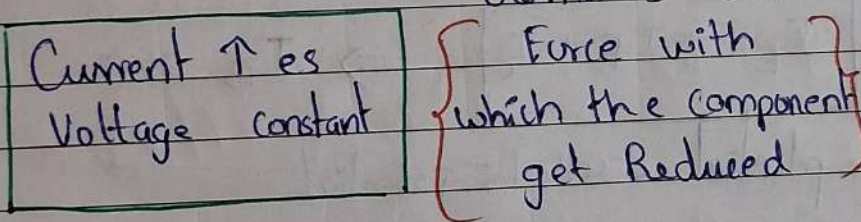
## Uses

- Mostly used in Reverse Bias condition

In R.B (Reverse Bias) condition current increases  $\uparrow$  voltage remains constant






\* Doping - Inserting non-semiconductor (P-type substrate)

$$V_{ED} > V_{Knee Voltage}$$



21/10/24

TRANSISTOR WORKING

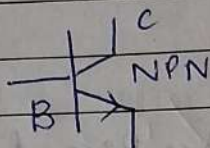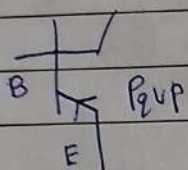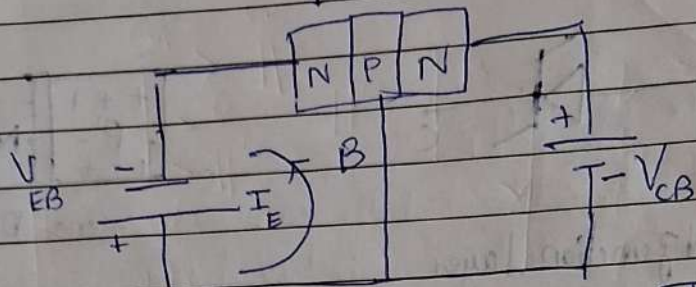

$J_1 \rightarrow$  Emitter junction  
(or)

Emitter Diode

$\rightarrow V_{EB} \rightarrow E_B$

$\Rightarrow$  Cap

$J_2 \rightarrow$  Collector junction

$\rightarrow V_{CB} \rightarrow R_B$

\*

$$\rightarrow \boxed{I_E \approx I_B + I_C} \Rightarrow I_B \approx 0$$


$\Rightarrow$  S

$\rightarrow$  Base potential < collector potential

$$\boxed{V_{EB} < V_{CB}}$$

$\Rightarrow$  Gr

Emitter voltage < collector voltage

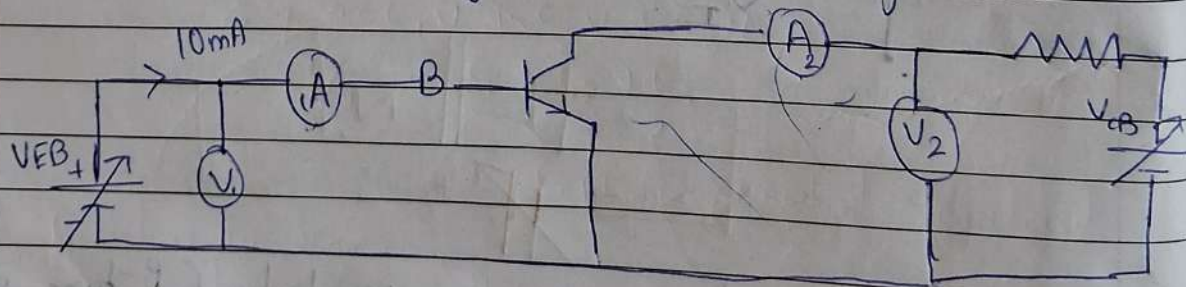

$V_{CB} \uparrow \rightarrow I_{ES}$

$V_{EB} >$  knee voltage

Emitter junction starts conducting.

\* R  
\* L

\* E  
\* B  
\* C



\* E



- \* Emitter layer is medium
- \* Base layer is thin layer
- \* Collector layer is bigger

Page No.

Date

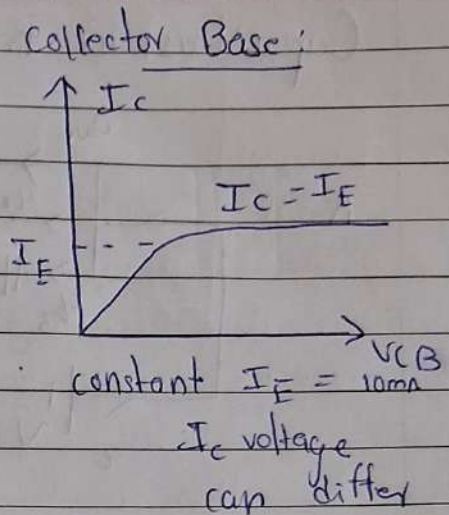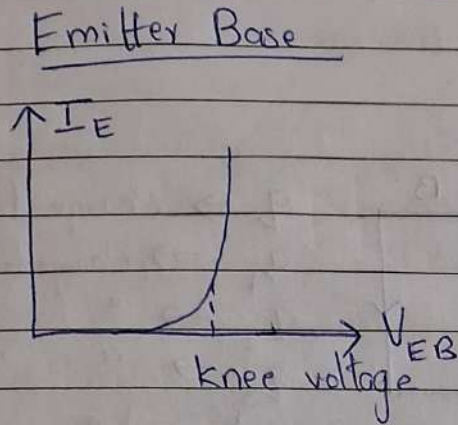

⇒ Capacitors - It is a two-terminal electrical devices that can store energy in the form of an electric charge


- \* In our everyday life we use (220-240V)

⇒ Stabilizers :- Stabilizers Voltage as well is an electrical device that delivers constant voltage to electrical appliances and electronics

⇒ Inductors :- A passive two-terminal electrical component that stores energy in a magnetic field when electric current flows through it
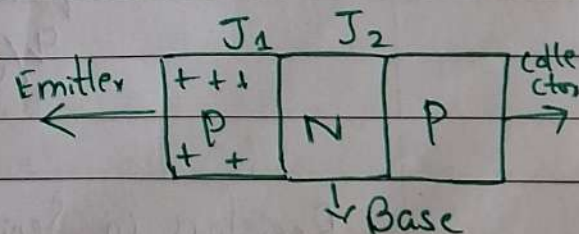
## TRANSISTOR

- \* Revolution of whole electric field
- \* LED - Light emitting diode




- \* Emitter heavily doped E - Emitter
- \* Base medium doped C - Collector
- \* Collector lightly doped B - Base


\* Emitter layer is bigger when compared to Base layer



## Capacitors in Parallel:

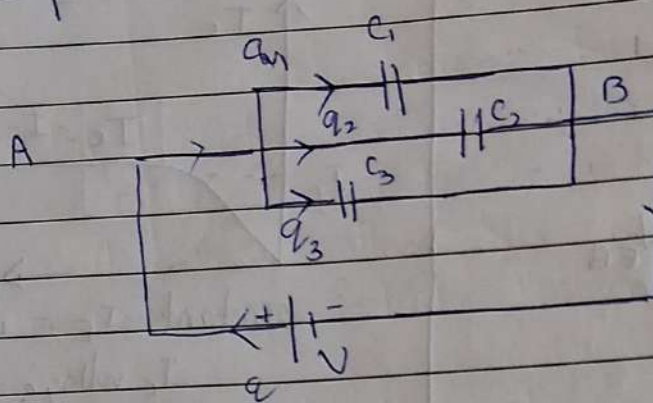

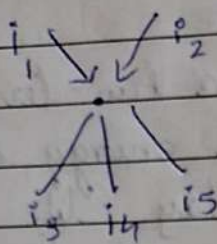$q \rightarrow$  charge from  $V$   
 $q_1 \rightarrow$  charge from  $C_1$   
 $q_2 \rightarrow$  " "  $C_2$   
 $q_3 \rightarrow$  " "  $C_3$   
 at point A apply KCL  
 $q = q_1 + q_2 + q_3$



KCL

algebraic sum of current meeting at a point is zero

$$\Rightarrow q = q_1 + q_2 + q_3$$

we know

$$C = q/V$$

$$\Rightarrow q = CV$$

$$\therefore q_1 = C_1 V$$

$$q_2 = C_2 V$$

$$q_3 = C_3 V$$

$$\therefore q = C_1 V + C_2 V + C_3 V$$

$$q/V = C_1 + C_2 + C_3$$

$C_{eff}$  (equivalent capacitance)

Resistors in Series


= Capacitance in parallel

$$C_{eff} = C_1 + C_2 + C_3$$

$\therefore C \uparrow \Rightarrow q \uparrow \text{ as } V \downarrow \text{ as}$



## Capacitors in Series

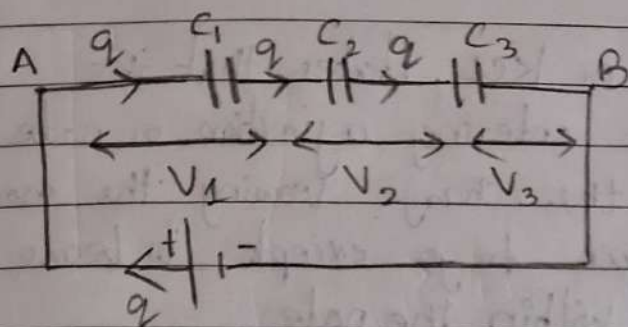

$$\Rightarrow C = q/V, V = q/C$$

$$\Rightarrow V_1 = q/C_1, V_2 = q/C_2$$

$$V_3 = q/C_3$$

$V_1$  = voltage across  $C_1$

$V_2$  = voltage across  $C_2$

$V_3$  = voltage across  $C_3$

$\Rightarrow$  Applying KVL Law

Sum of all voltage in a given closed circuit is equal to zero



$$V = V_1 + V_2 + V_3$$

$$V = q/C_1 + q/C_2 + q/C_3$$

$$V = q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\therefore V/q = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = 1/C_{\text{eff}}$$

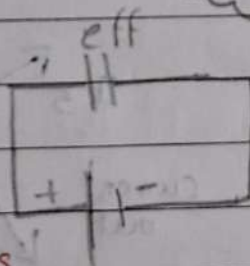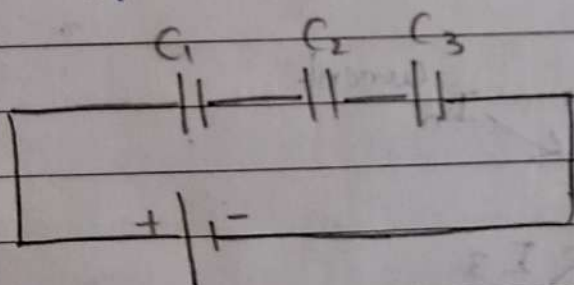effective (or)  
equivalent  
capacitance



$C \downarrow$  as  $q \downarrow$  as  $V \uparrow$  as

$\Rightarrow$  voltage divider circuit

\* In series we can store more charges

## KCL Law


Kirchoff's Current law or KCL, states that the total current or charge entering a junction or node is exactly equal to the charge leaving the node as it has no other place to go except to leave as no charge is lost within the node.

In other words the algebraic sum of All the currents entering and leaving a node must be equal to zero.

$$I(\text{exiting}) + I(\text{entering}) = 0$$

This idea by kirchoffs is commonly known as the conservation of charge.






Kirchoff's Current Law.

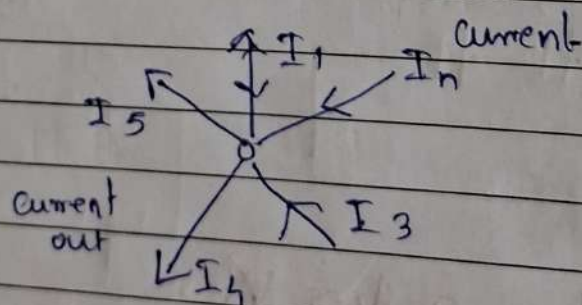

$$I_1 + I_2 + I_3 (-I_4 + -I_5) = 0$$



# FET (Field Effect Transistors)

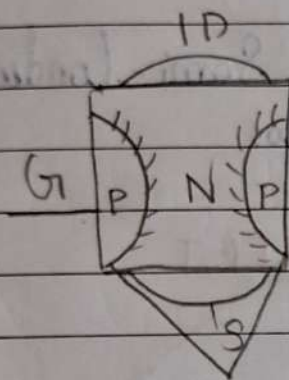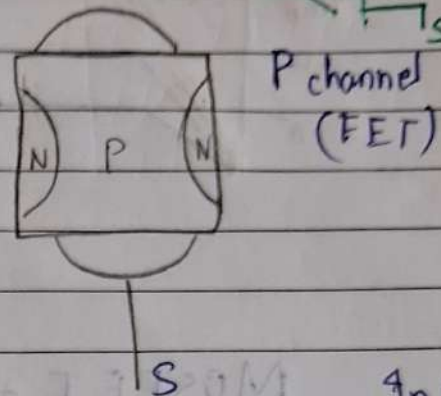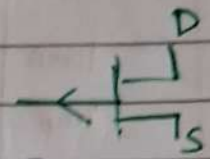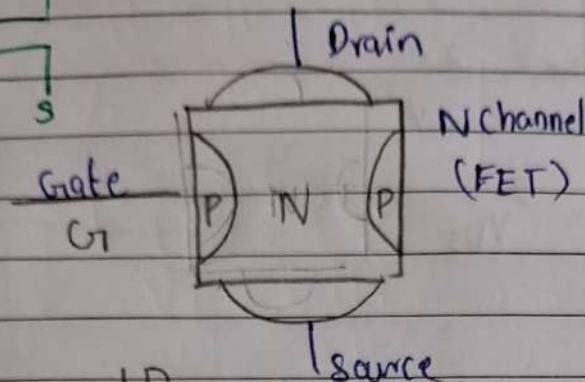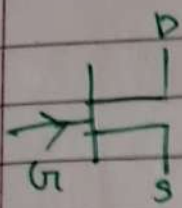


→ In F. Biasing condition  
the depletion layer width  
is not going to change

In R.B

The depletion  
layer is

⇒ Nchannel Depletion  
(FET)

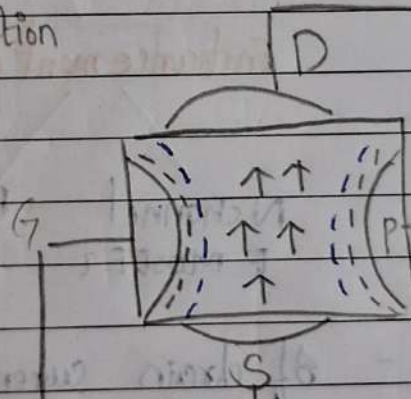


Voltage Controlled  
Device


Not Bipolar  
But unidirectional


$V_{GS}$

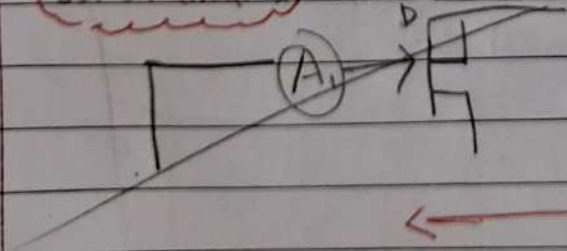Work on  
R. Biasing  
Based on  $V_{GS}$  voltage  
the current flow is  
determined




FET is  
voltage  
controlled

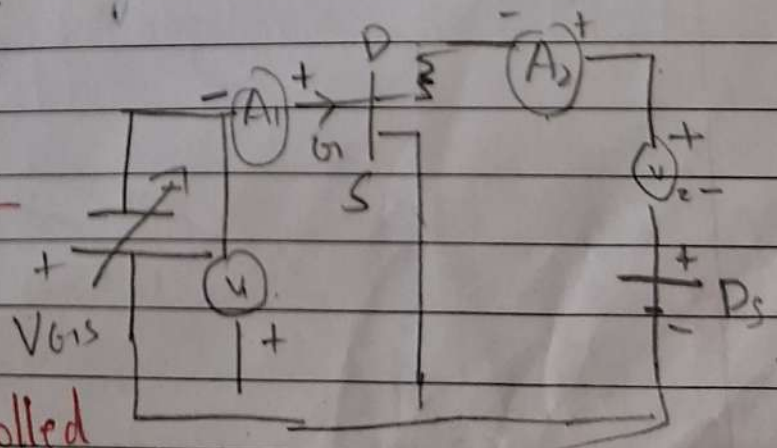

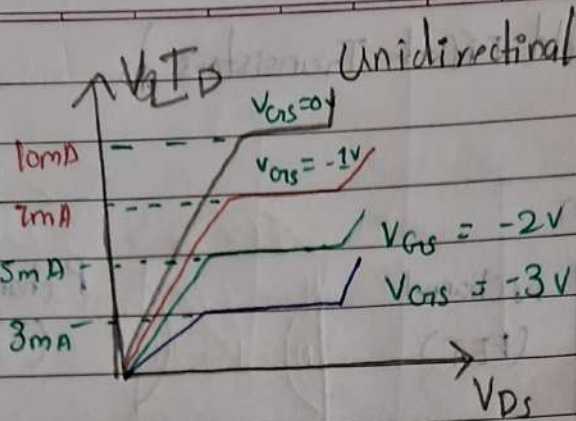

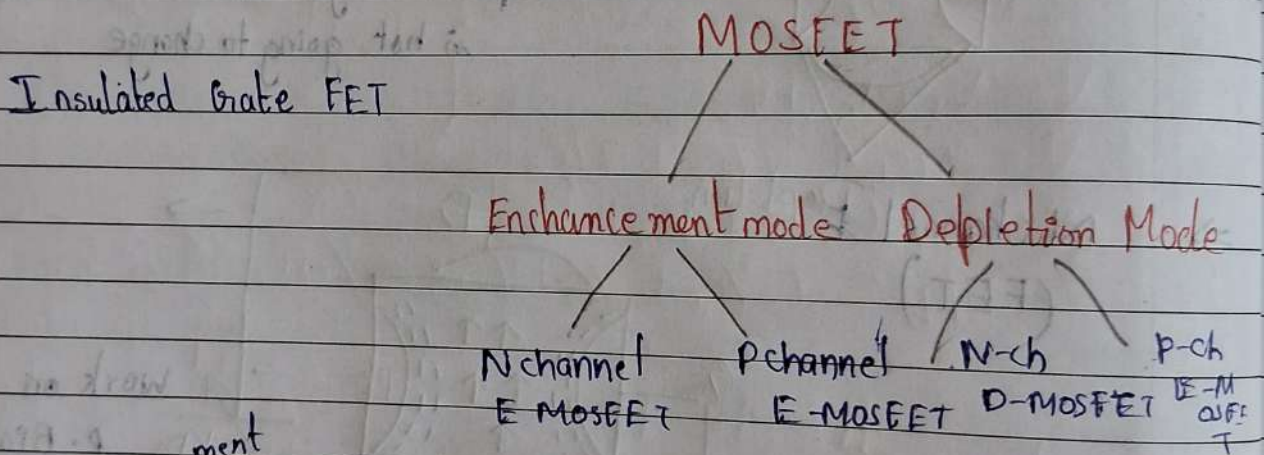23/10/2020 MOSFET - Metal Oxide Semi-Conductor Field Effect Transistor




Enhancement Mode :- If drain current  $I_{DS}$  based on Gate + Source voltage

Depletion Mode :- If drain current  $I_{DS}$




N type is doped

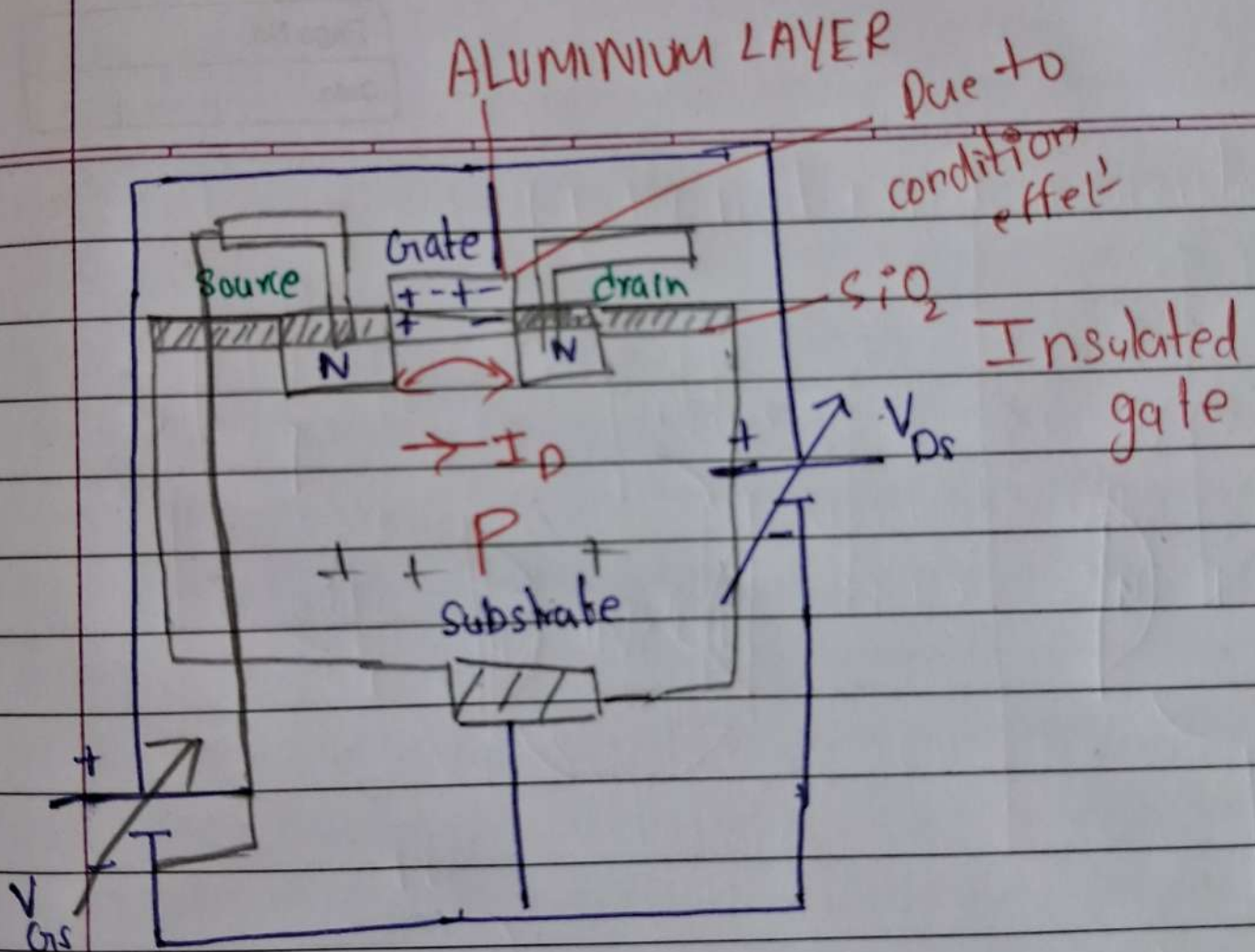

N channel

E - MOSFET

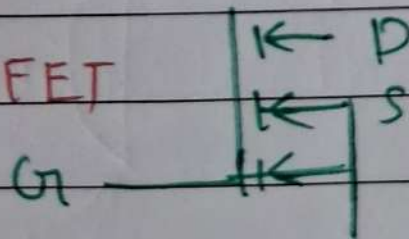

$I_D$

$$V_{GS} = 3V$$

$$V_{GS} =$$

$$V_{GS} =$$

$$V_{GS} =$$