

Electrical and Electromechanical Computer Science


Current \rightarrow voltage \rightarrow Resistance

$$V = I/R$$

Band Colours


Tolerance values

Black - $0, 10^0$	silver - $\pm 10\%$	NA
Brown - $1, 10^1$		± 1
Red - $2, 10^2$		± 2
Orange - $3, 10^3$		NA
Yellow - $4, 10^4$		NA
Green - $5, 10^5$	blue - $6 - 10,000$	$\pm 0.5\%$
Violet - $6, 10^6$		$\pm 0.25\%$
Grey - $7, 10^7$	$1,000,000$	$\pm 0.10\%$
White - $8, 10^8$	$1,000,000,000$	NA $\pm 0.05\%$
Gold - $9, 10^9$	$\pm 5\%$ $1,000,000,000$	NA

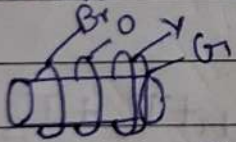

Brown - 1, Orange 3, Yellow - 10^4 , Gold - ± 5

$$13 \times 10^4 \pm 5$$

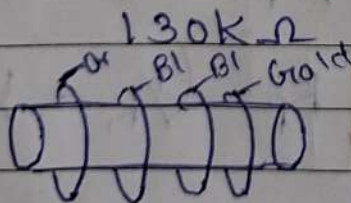


$$30 \times 10^0 \pm 5$$

$$= 30 \Omega \pm 5 //$$

Resistors in Series

Current - remains Same
Voltage - changes

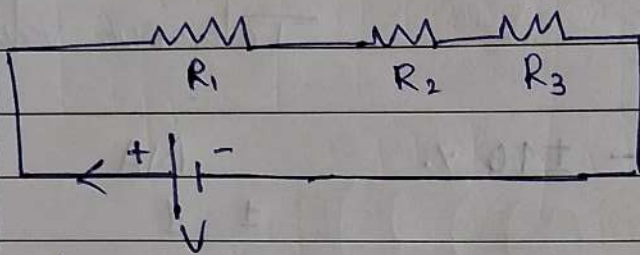

$$V = V_1 + V_2 + V_3$$


$$IR_s = IR_1 + IR_2 + IR_3$$

$$IR_s = I(R_1 + R_2 + R_3)$$

$$\Rightarrow R_s = R_1 + R_2 + R_3$$

Resistors in Parallel

Current - changes
Voltage - Remains Same

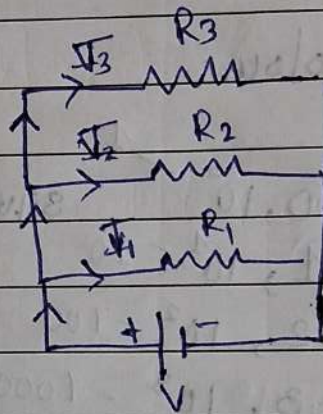

$$I \neq V = I/R$$

$$I = V/R$$

$$V/R_1 = I_1$$

$$V/R_2 = I_2$$

$$V/R_3 = I_3$$

$$I = I_1 + I_2 + I_3$$

$$V/R_p = V/R_1 + V/R_2 + V/R_3$$


$$V/R_p = V(1/R_1 + 1/R_2 + 1/R_3)$$

$$R_p = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

07/5/10

Diodes

PN junction diode

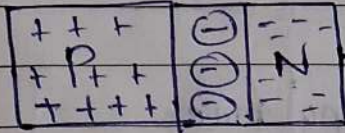


P and N subscript

particles

P- Holes containing protons, relectrons and neutrons, whereas as

N- ~~A~~ Electron are negatively charged

* Holes are heavy than electrons

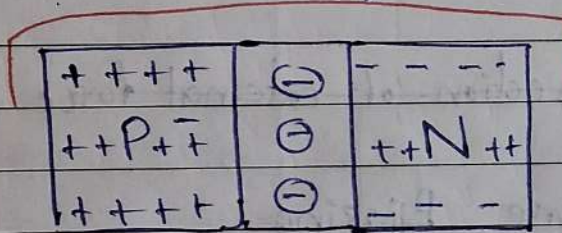

Barrier potential

(due to dis. electrons + holes stop move)

PN junction


* opposite. poles attract each other

pulling

* positive carriers are heavy compared to electrons


* Electrons move faster

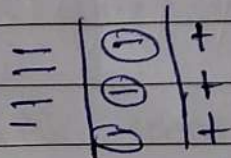Re combination of electrons \rightarrow Biasing





P type \rightarrow Anode

N type \rightarrow Cathode

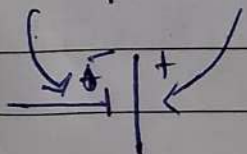


electrostatic field

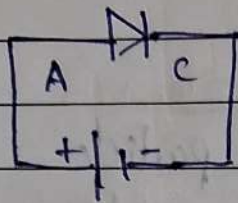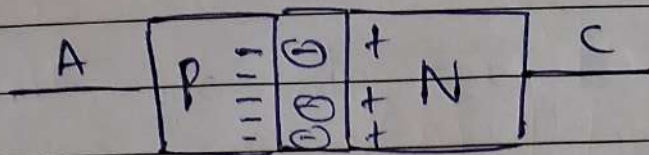


Connection of external force

Electron + holes is called Biasing

Forward Biasing

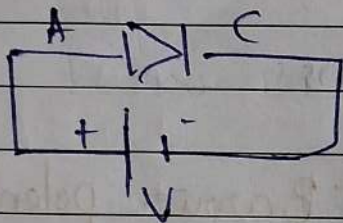

Connection of external force

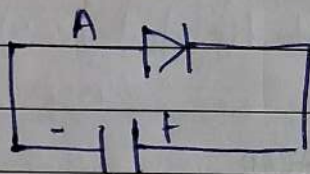


Reverse Biasing :

(-) $P \rightarrow A$


(+) $N \rightarrow C$

Forward Bias:

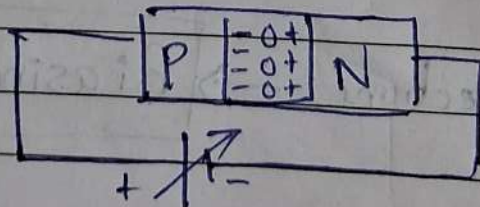

Silicon material (Si) $V_{Bp} \rightarrow 0.7v$

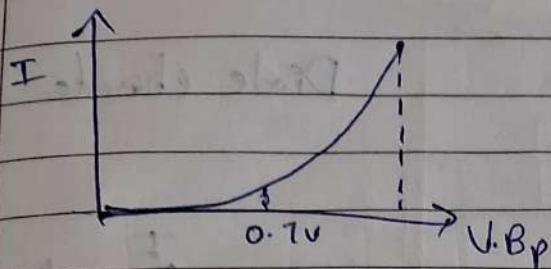Germanium " " (Ge) $V_{Bp} \rightarrow 0.3v$




Diode is unidirectional

here I - movement of both carriers
so it is called as Bipolar device
 \therefore diode is bipolar device

The Direction of current (I)

Anode to cathode (so it is unidirectional)

Reverse Biasing

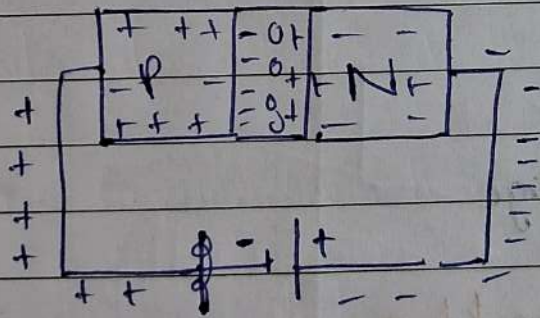


\times -ve plate \rightarrow p layer majority \rightarrow +ve attract

+ve plate \rightarrow N layer majority \rightarrow -ve attract



\therefore No carriers crossing the junction

$\therefore I = 0$

⇒ At one stage

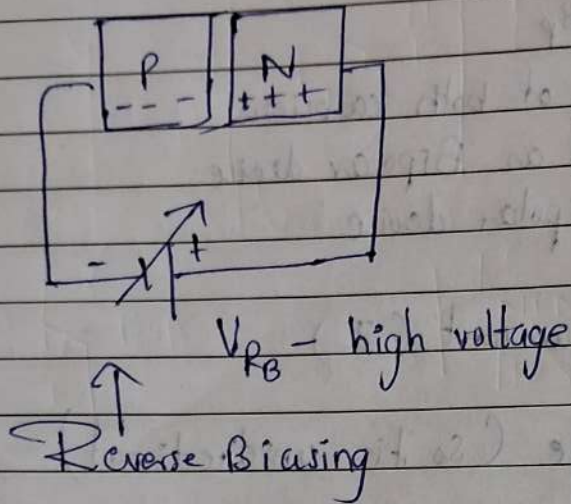

Diode character

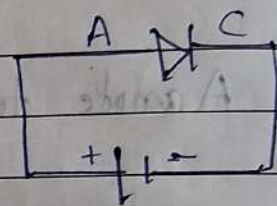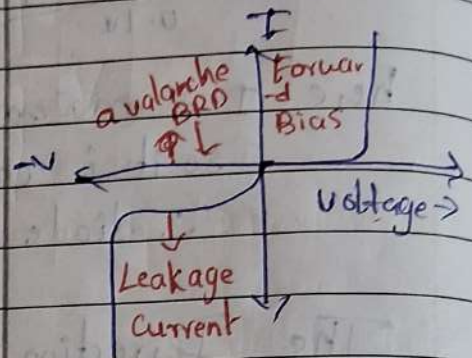

due to high potential
→ high force moving the charges



electrons (-) → N layer
protons (+) → P layer

∴ due to this function damage
This damage is called
Avalanche Breakdown

CHARACTERISTICS



Zener Diode

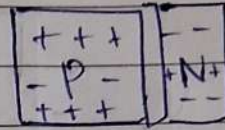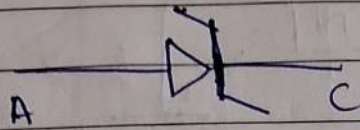




Zener Diode

- Very thin PN junction layer
- Zener diode is Bi directional

Uses

- Mostly used in Reverse Bias condition

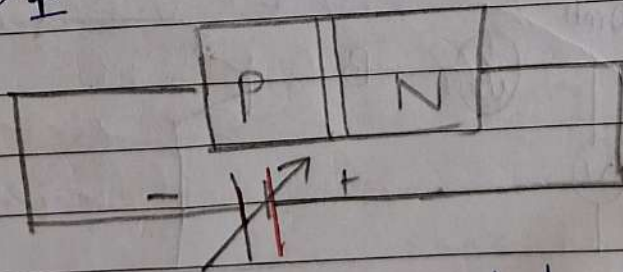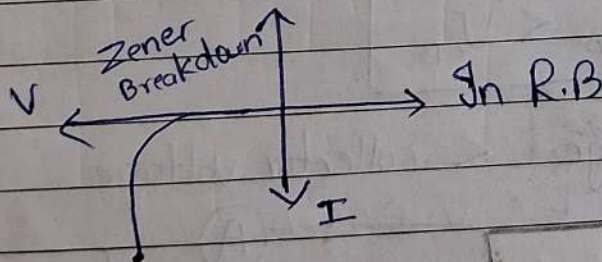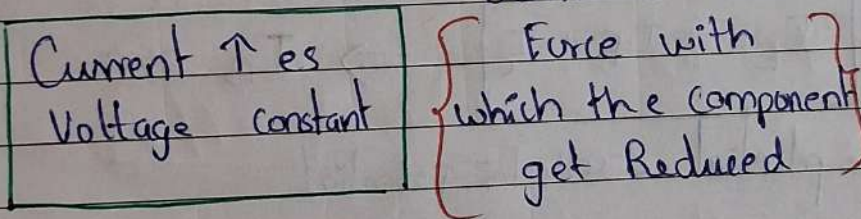In R.B (Reverse Bias) condition current increases \uparrow voltage remains constant






* Doping - Inserting non-semiconductor (P-type substrate)

$$V_{ED} > V_{Knee Voltage}$$

21/10/24

TRANSISTOR WORKING

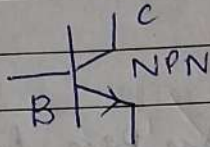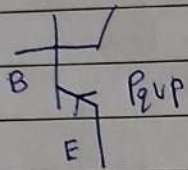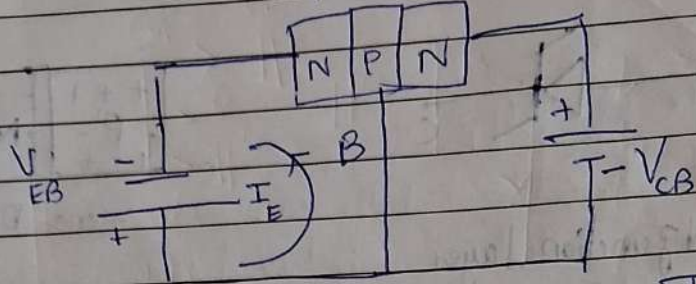

$J_1 \rightarrow$ Emitter junction
(or)

Emitter Diode
 $\rightarrow V_{EB} \rightarrow E \rightarrow B$


$J_2 \rightarrow$ Collector junction
 $\rightarrow V_{CB} \rightarrow C \rightarrow B$

$$\rightarrow \boxed{I_E \approx I_B + I_C} \Rightarrow I_B \approx 0$$

\rightarrow Base potential < collector potential

$$\boxed{V_{EB} < V_{CB}}$$

Emitter voltage < collector voltage

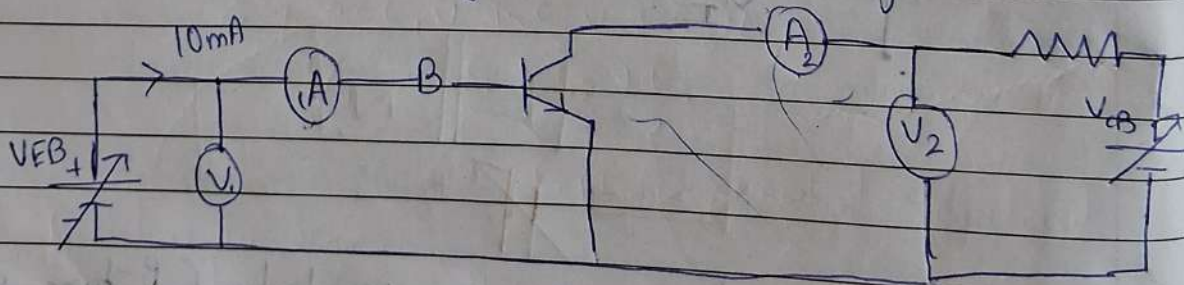

$$V_{CB} \uparrow \rightarrow I_{ES} \rightarrow I_{CS}$$



$V_{EB} >$ knee voltage

Emitter junction starts conducting.

- * Emitter layer is medium
- * Base layer is thin layer
- * Collector layer is bigger

Page No.

Date

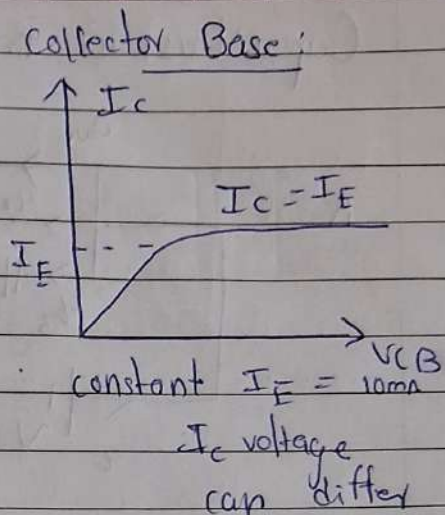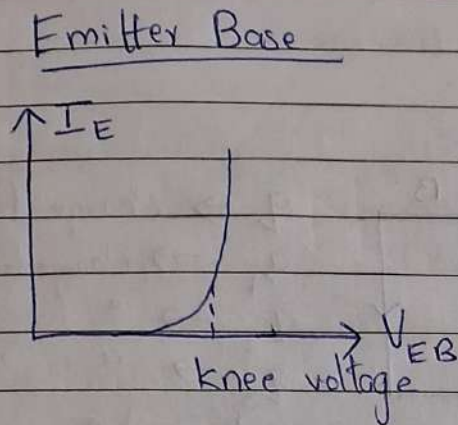

⇒ Capacitors - It is a two-terminal electrical devices that can store energy in the form of an electric charge


- * In our everyday life we use (220-240V)

⇒ Stabilizers :- Stabilizers Voltage as well is an electrical device that delivers constant voltage to electrical appliances and electronics

⇒ Inductors :- A passive two-terminal electrical component that stores energy in a magnetic field when electric current flows through it

TRANSISTOR

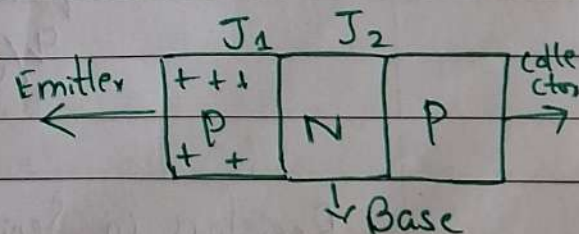
- * Revolution of whole electric field
- * LED - Light emitting diode




- * Emitter heavily doped E - Emitter
- * Base medium doped C - Collector
- * Collector lightly doped B - Base

* Emitter layer is bigger when compared to Base layer

Capacitors in Parallel:

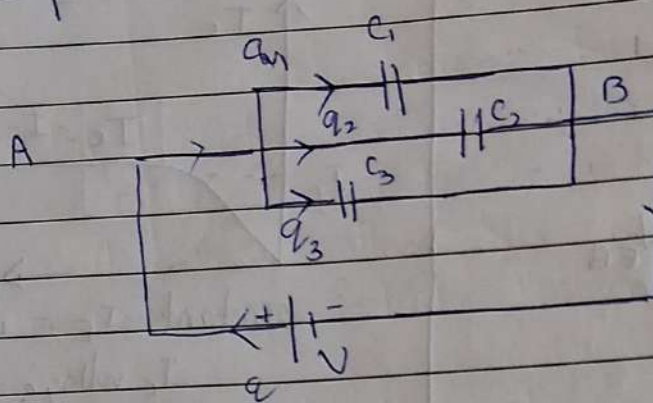

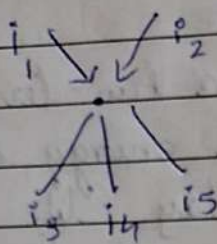$q \rightarrow$ charge from V
 $q_1 \rightarrow$ charge from C_1
 $q_2 \rightarrow$ " " C_2
 $q_3 \rightarrow$ " " C_3
 at point A apply KCL
 $q = q_1 + q_2 + q_3$



KCL
 algebraic sum of
 current meeting at
 a point is zero

$$\Rightarrow q = q_1 + q_2 + q_3$$

we know

$$C = q/V$$

$$\Rightarrow q = CV$$

$$\therefore q_1 = C_1 V$$

$$q_2 = C_2 V$$

$$q_3 = C_3 V$$

$$\therefore q = C_1 V + C_2 V + C_3 V$$

$$q/V = C_1 + C_2 + C_3$$

C_{eff} (equivalent capacitance)


Resistors in Series

= Capacitance in parallel

$$C_{eff} = C_1 + C_2 + C_3$$

$\therefore C \uparrow \Rightarrow q \uparrow \text{ as } V \downarrow \text{ as}$

Capacitors in Series

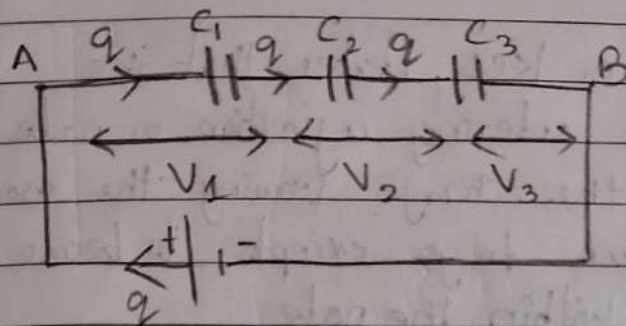

$$\Rightarrow C = q/V, V = q/C$$

$$\Rightarrow V_1 = q/C_1, V_2 = q/C_2$$

$$V_3 = q/C_3$$

V_1 = voltage across C_1

V_2 = voltage across C_2

V_3 = voltage across C_3

\Rightarrow Applying KVL Law

Sum of all voltage in a given closed circuit is equal to zero



$$V = V_1 + V_2 + V_3$$

$$V = q/C_1 + q/C_2 + q/C_3$$

$$V = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\therefore V/q = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = 1/C_{\text{eff}}$$

effective (or)
equivalent
capacitance

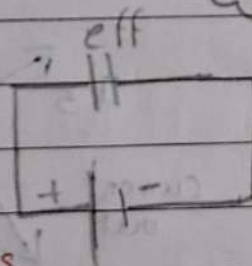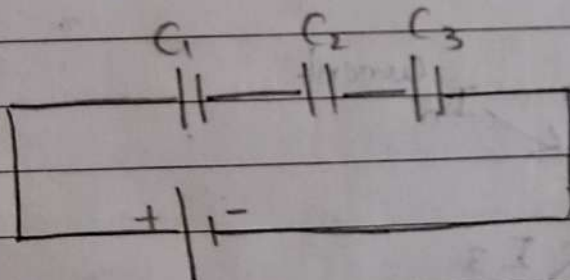

$C \downarrow$ as $q \downarrow$ as $V \uparrow$ as

\Rightarrow voltage divider circuit

* In series we can store more charges

KCL Law


Kirchoff's Current law or KCL, states that the total current or charge entering a junction or node is exactly equal to the charge leaving the node as it has no other place to go except to leave as no charge is lost within the node.

In other words the algebraic sum of All the currents entering and leaving a node must be equal to zero.

$$I(\text{exiting}) + I(\text{entering}) = 0$$






This idea by kirchoffs is commonly known as the conservation of charge.

Kirchoff's Current Law.

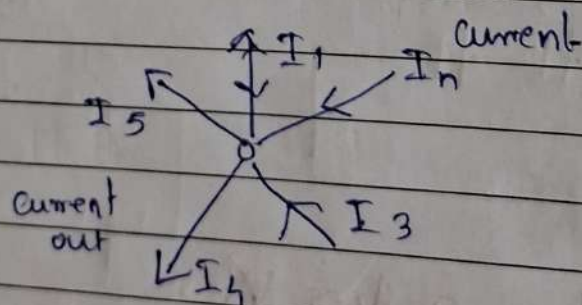

$$I_1 + I_2 + I_3 (-I_4 + -I_5) = 0$$

FET (Field Effect Transistors)

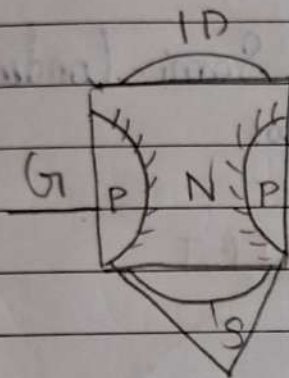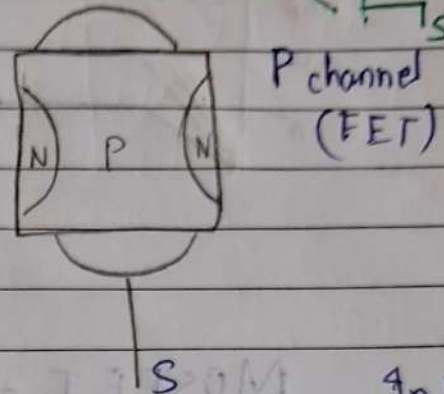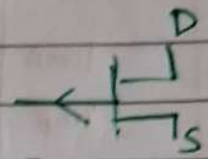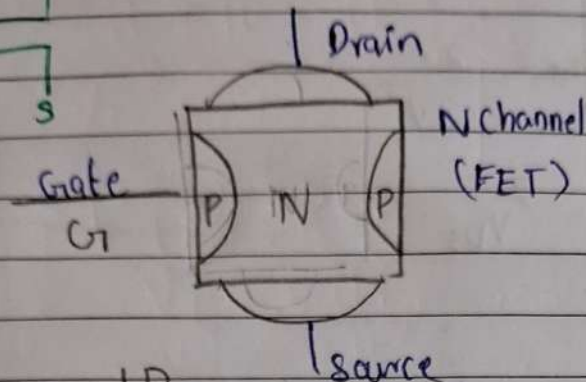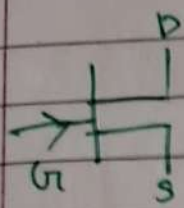


→ In F. Biasing condition
the depletion layer width
is not going to change

In R.B

The depletion
layer is

⇒ Nchannel Depletion
(FET)

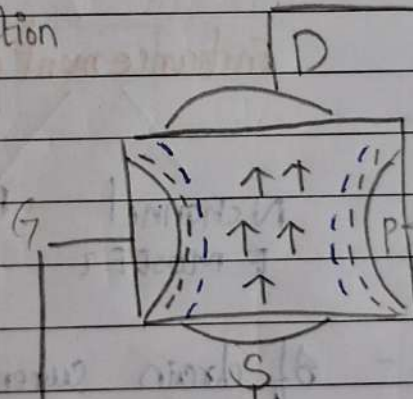


Voltage Controlled
Device


Not Bipolar
But unidirectional


V_{GS}

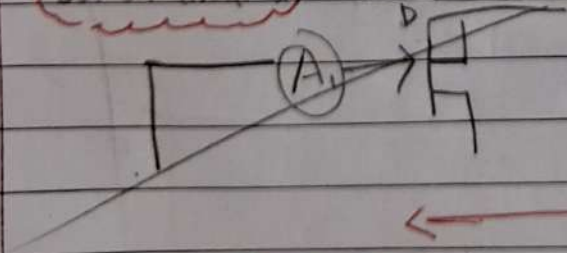work on
R. Biasing
Based on V_{GS} voltage
the current flow is
determined




FET is
voltage
controlled

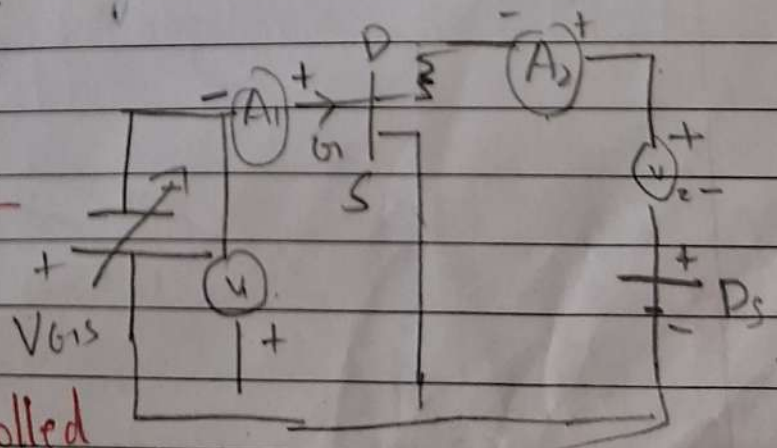

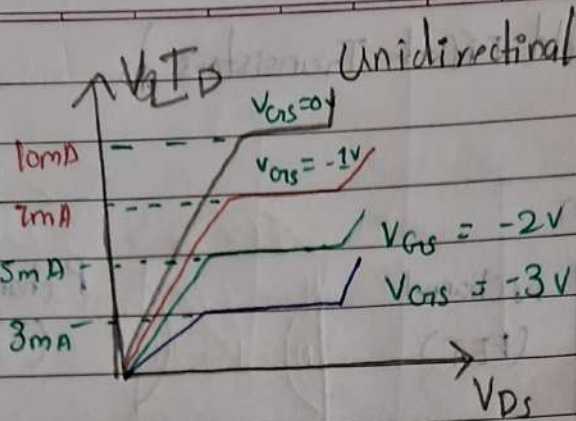

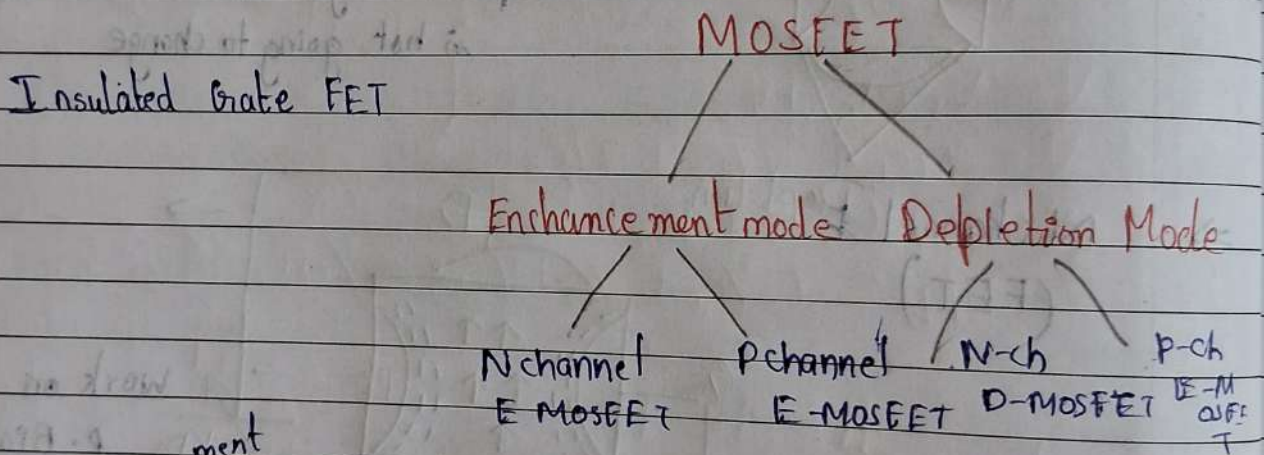
23/10/2020 MOSFET - Metal Oxide Semi-Conductor Field Effect Transistor



Enhancement Mode :- If drain current \uparrow es based on Gate + Source voltage


Depletion Mode :- If drain current \uparrow es

N type is doped

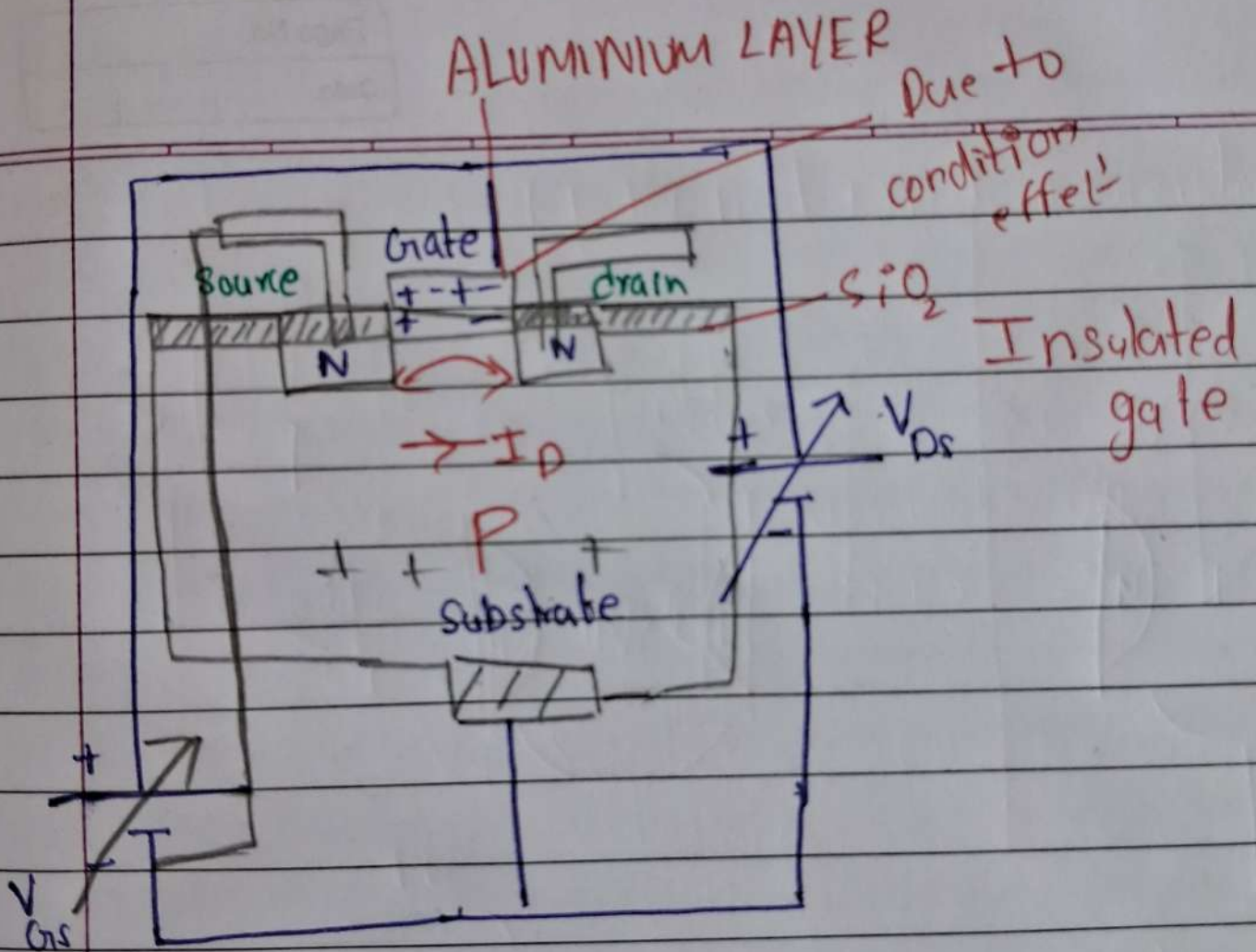

N channel

E - MOSFET

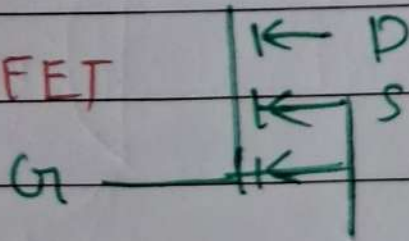

I_D

$$V_{GS} = 3V$$

$$V_{GS} =$$

$$V_{GS} =$$

$$V_{GS} =$$